

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Science**

6.622 Power Electronics

Issued: February 6, 2023

Problem Set 0

Due: February 13, 2023

---


Reading: KPVS Chapters 1 and 2

---

### **Problem 0.1**

Figure 0.1 shows the circuit diagram of a magnetic stimulator made by an international biomedical electronics company. The pulsed magnetic field generated by the transducer coil (represented by the inductor) can be used in a variety of medical treatments including nerve stimulation. The capacitor is precharged to a Voltage  $V_x$  between 0 and 1000 V, and then at  $t = 0$  the switch  $S$  is closed to trigger the magnetic pulse.

- a. Calculate the following assuming that the switch  $S$  and the diode  $D$  are ideal:
  1. The time response of the coil current after the switch  $S$  is closed, as a function of the precharge voltage  $V_x$ . (Some types of stimulation require a field with a fast rise time and a slow fall time.)
  2. The peak coil current  $i_{coil}$  for  $V_x = 900$  V.
  3. The time  $t_1$  at which diode  $D$  turns on.
  4. The energy dissipated in the resistor for  $V_x = 900$  V.
- b. Using any time-domain simulation tool you want (e.g. LTSPICE, PSIM, Simulink, etc.), simulate the circuit for 1 ms after the switch is closed. Assume that  $V_c = 900$  V when switch  $S$  is closed, focusing on the coil current and capacitor voltage. Note that the LTSPICE simulator can be obtained for free at:  
<http://www.linear.com/design-tools/software/#LTspice>
- c. Considering that the system of Fig. 1.2 may be thought of as a switched *linear* system, can you predict how the coil current and capacitor voltage waveforms will scale in amplitude and/or time as the initial charge voltage  $V_c$  changes? Verify your prediction by running another simulation with an initial voltage  $V_c = 450$  V.

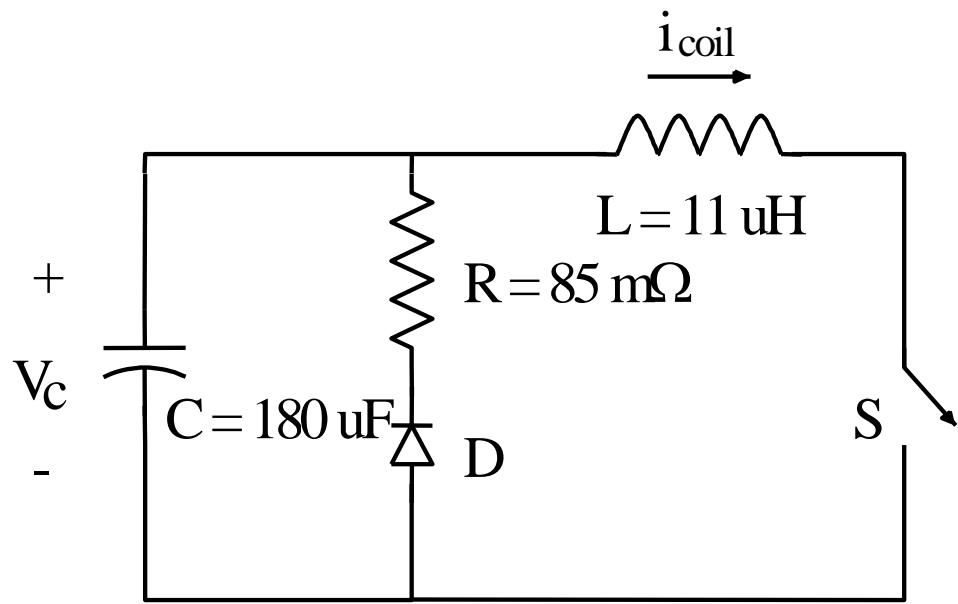

**Figure 0.1** Schematic of the magnetic stimulator circuit. The capacitor voltage  $V_C$  is precharged to 900 V when the switch  $S$  is closed.

MIT OpenCourseWare

<https://ocw.mit.edu>

6.622 Power Electronics

Spring 2023

For information about citing these materials or our Terms of Use, visit: <https://ocw.mit.edu/terms>